

CMOS Operational Amplifier Design and Optimization via Geometric Programming

Maria del Mar Hershenson

Stephen Boyd, Thomas H. Lee

Electrical Engineering Department
Stanford University



July 28, 1997



CMOS Op-Amp Design and Optimization via G.P.

Main Idea

- Many op-amp design problems can be cast as a special type of **convex optimization problems**.
- Such problems can appear very difficult, but can be solved **very efficiently** by recently developed interior-point (IP) methods.



CMOS Op-Amp Design and Optimization via G.P.

Outline

- Convex Optimization
- Posynomial Functions
- Geometric Programming
- Application to a Two-Stage Operational Amplifier
- Results
- Conclusions




Convex Optimization

minimize $f_0(x)$

subject to $f_1(x) \leq 0, \dots, f_L(x) \leq 0, Ax = b$

- $x \in \mathbb{R}^n$ is optimization variable
- f_i are **convex**:
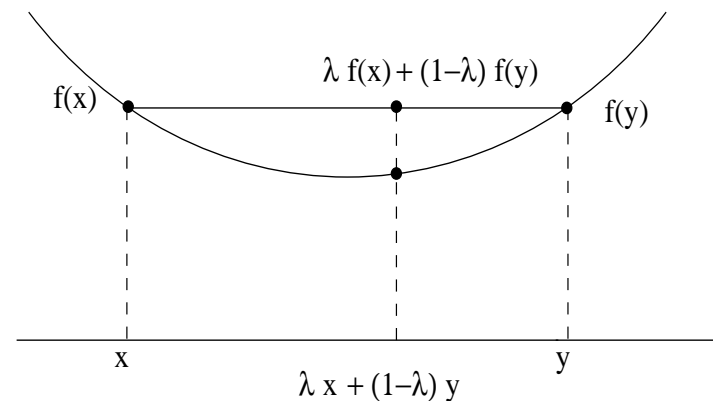
$$\begin{aligned} &\text{for } 0 \leq \lambda \leq 1, \\ &f_i(\lambda x + (1 - \lambda)y) \\ &\leq \lambda f_i(x) + (1 - \lambda)f_i(y) \end{aligned}$$





Convex Optimization problems are fundamentally tractable

- computation time is small, grows gracefully with problem size and required accuracy
- large problems solved quickly in practice
- what “solve” means:
 - find **global** optimum within a given tolerance, or,
 - find **proof** (certificate) of infeasibility



Posynomial Functions

$$f(x_1, \dots, x_n) = \sum_{k=1}^t c_k x_1^{\alpha_{1k}} x_2^{\alpha_{2k}} \dots x_n^{\alpha_{nk}}$$

- f is a real-valued function of n real, positive variables $x = (x_1, x_2, \dots, x_n)$.
- $c_j \geq 0$ and $\alpha_{ij} \in \mathbb{R}$.
- If $t = 1$, f is called a *monomial* function.
- If f is a posynomial function, $\frac{1}{f}$ is called an *inverse-posynomial* function.
- Posynomials are *closed under sums, products, and nonnegative scaling*.



Posynomial Functions: Examples

- **Posynomial**

$$f_1 = 3x_1^{-0.3} + x_2^{1.3} x_3^{4.1} x_5 + .25x_1^{14} x_3^{-0.8} x_4^2$$

- **Monomial**

$$f_2 = .25x_1^{14} x_3^{-0.8} x_4^2$$

- **Inverse Posynomial**

$$f_3 = \frac{1}{3x_1^{-0.3} + x_2^{1.3} x_3^{4.1} x_5 + .25x_1^{14} x_3^{-0.8} x_4^2}$$



CMOS Op-Amp Design and Optimization via G.P.

Geometric Programming

$$\begin{aligned} &\text{minimize} && f_0(x) \\ &\text{subject to} && f_i(x) \leq 1, \quad i = 1, \dots, m \\ & && g_i(x) = 1, \quad i = 1, \dots, p \\ & && x_i > 0, \quad i = 1, \dots, n \end{aligned}$$

where f_i are *posynomial* functions and g_i are *monomial* functions.

The objective function $f_0(x)$ can be monomial or posynomial.



Geometric Programming

We can


- *minimize* any posynomial or monomial function
- or *maximize* any inverse-posynomial or monomial function

subject to

- *upper-bounded* posynomial functions
- *lower-bounded* inverse-posynomial functions
- *upper and/or lower-bounded* monomial functions.



Two-Stage Operational Amplifier

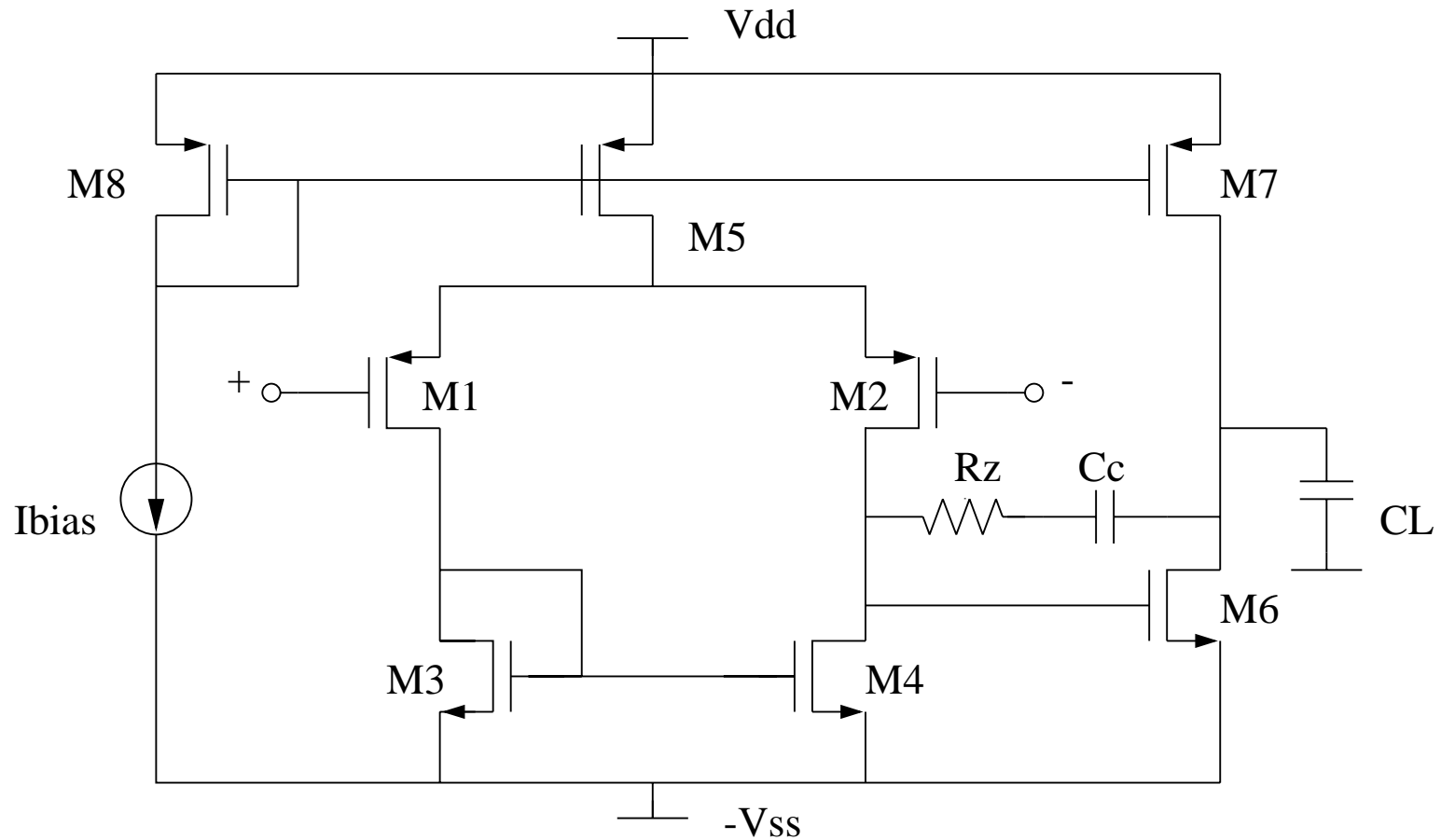



Dimension Constraints

- Minimum Device Sizes → **Monomial**

$$L_i \geq L_{\min} \quad \text{and} \quad W_i \geq W_{\min}$$


- Area → **Posynomial**

$$\text{Area} = \alpha_1 C_c + \alpha_2 \sum_i W_i L_i.$$

- Systematic Input Offset Voltage → **Monomial**

$$\frac{(W/L)_3}{(W/L)_6} = \frac{1}{2} \frac{(W/L)_5}{(W/L)_7}$$
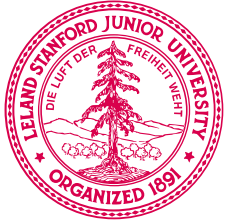
$$\frac{(W/L)_4}{(W/L)_6} = \frac{1}{2} \frac{(W/L)_5}{(W/L)_7}.$$



Bias Conditions

- Additional variables \rightarrow **Monomial**

$$I_5 = \frac{W_5 L_8}{L_5 W_8} I_{\text{bias}} \quad I_7 = \frac{W_7 L_8}{L_7 W_8} I_{\text{bias}} \quad I_1 = \frac{I_5}{2}$$

- Transistors in saturation \rightarrow **Posynomial**
(Transistors M_1 and M_2)

$$\sqrt{\frac{I_1 L_3}{\mu_n C_{\text{ox}} / 2 W_3}} \leq V_{\text{cm},\text{min}} + V_{\text{ss}} - V_{\text{TP}} - V_{\text{TN}}$$

- Quiescent Power \rightarrow **Posynomial**

$$P = (V_{\text{dd}} + V_{\text{ss}}) (I_{\text{bias}} + I_5 + I_7)$$



Transfer Function (I)

- Open Loop Gain \rightarrow **Monomial**

$$A_v = \left(\frac{g_{m2}}{g_{o2} + g_{o4}} \right) \left(\frac{g_{m6}}{g_{o6} + g_{o7}} \right)$$

- 3-dB Cutoff Frequency \rightarrow **Monomial**

$$\omega_{3dB} = \frac{-g_{m1}}{A_v C_c}$$

- Unity Gain Frequency \rightarrow **Monomial**

$$\omega_c = \frac{g_{m1}}{C_c}$$




Transfer Function (II)

- Phase Margin Conditions \longrightarrow **Posynomial**

$$\frac{\omega_c}{p_2} + \frac{\omega_c}{z_1} \leq \frac{\pi}{2} - \text{PM}_{\min}$$

or
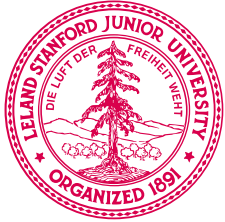
$$\frac{\omega_c}{p_2} + \frac{\omega_c}{p_3} \leq \frac{\pi}{2} - \text{PM}_{\min}$$




Slew Rate

- Slew Rate \rightarrow **Posynomial**

$$SR = \min \left(\frac{2I_1}{C_c}, \frac{I_7}{C_c + C_L} \right)$$

A constraint on slew rate can be written as
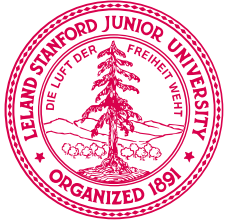
$$\frac{C_c}{2I_1} \leq \frac{1}{SR_{\min}}$$
$$\frac{C_c + C_L}{I_7} \leq \frac{1}{SR_{\min}}$$



Noise

- Input-referred Noise Spectral Density \rightarrow **Posynomial**

$$S_i(f) = \frac{v_{in}^2}{\Delta f} = \frac{2K_p}{C_{ox}W_1L_1} \left(1 + \frac{K_n\mu_nL_1^2}{K_p\mu_pL_3^2} \right) \frac{1}{f} + \frac{16kT}{3\sqrt{2\mu_pC_{ox}(W/L)_1I_1}} \left(1 + \sqrt{\frac{\mu_n(W/L)_3}{\mu_p(W/L)_1}} \right)$$


- Total Input-referred Noise \rightarrow **Posynomial**

$$\overline{v_{INT}^2} = \int_{f=0}^{f=f_n} S_i(f) df \approx \sum_{f=0}^{f=f_n} S_i(f) \Delta f$$




Other Constraints

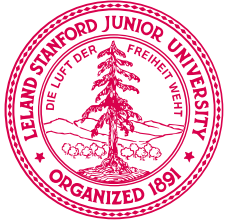- Symmetry \rightarrow **Monomial**
- Matching Conditions \rightarrow **Monomial**
- CMRR \rightarrow **Monomial**
- Gate Overdrive \rightarrow **Monomial**
- Poles and Zeros \rightarrow **Inverse-Posynomial**
- ...



CMOS Op-Amp Design and Optimization via G.P.


Optimal Trade-off Curves (I)

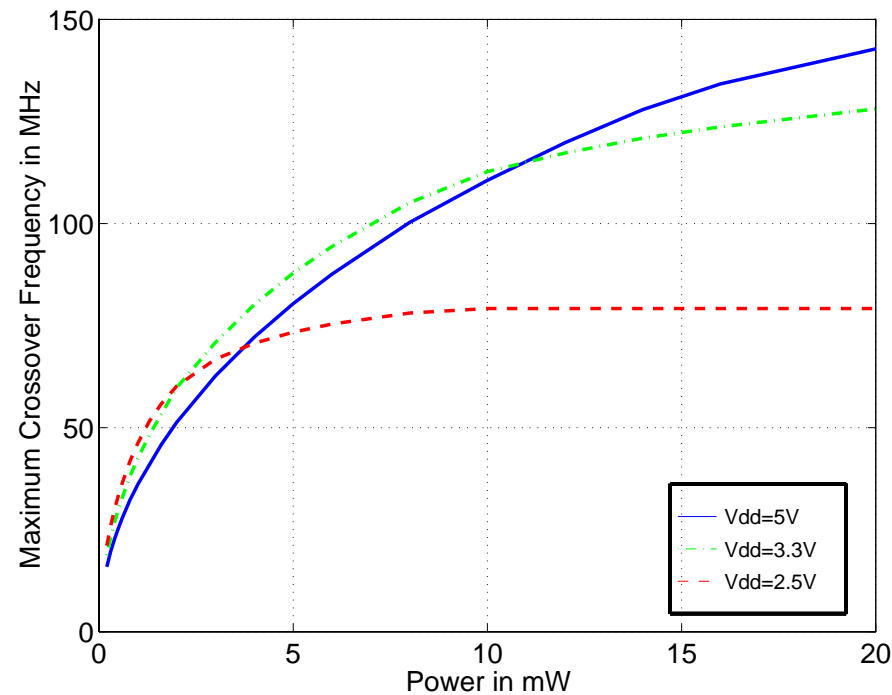

Unity gain bandwidth versus power for different supply voltages




Optimal Trade-off Curves (II)

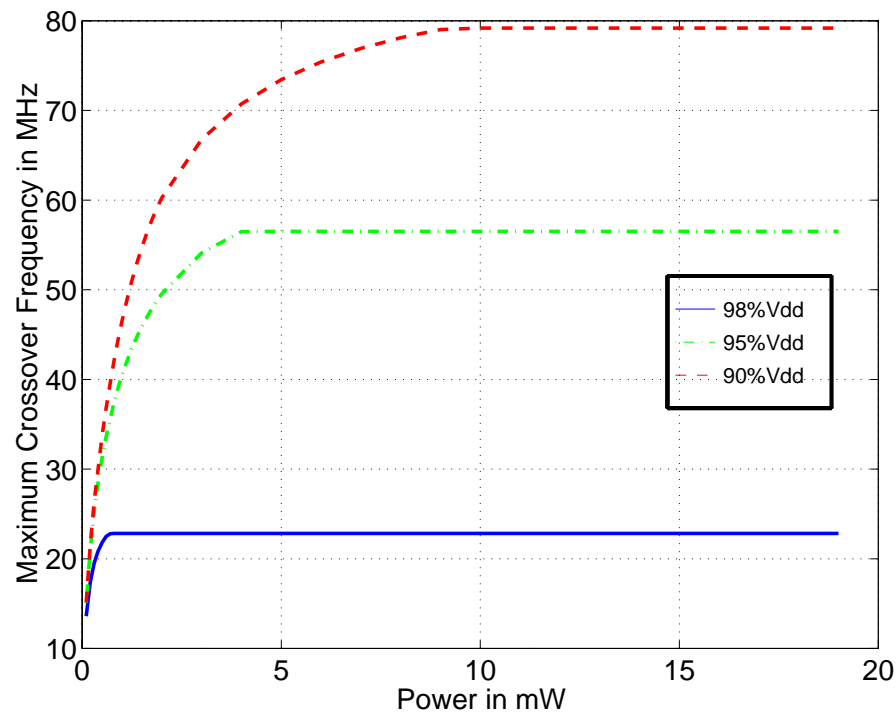

Maximum unity gain frequency versus power for different output voltage ranges




Optimal Trade-off Curves (III)

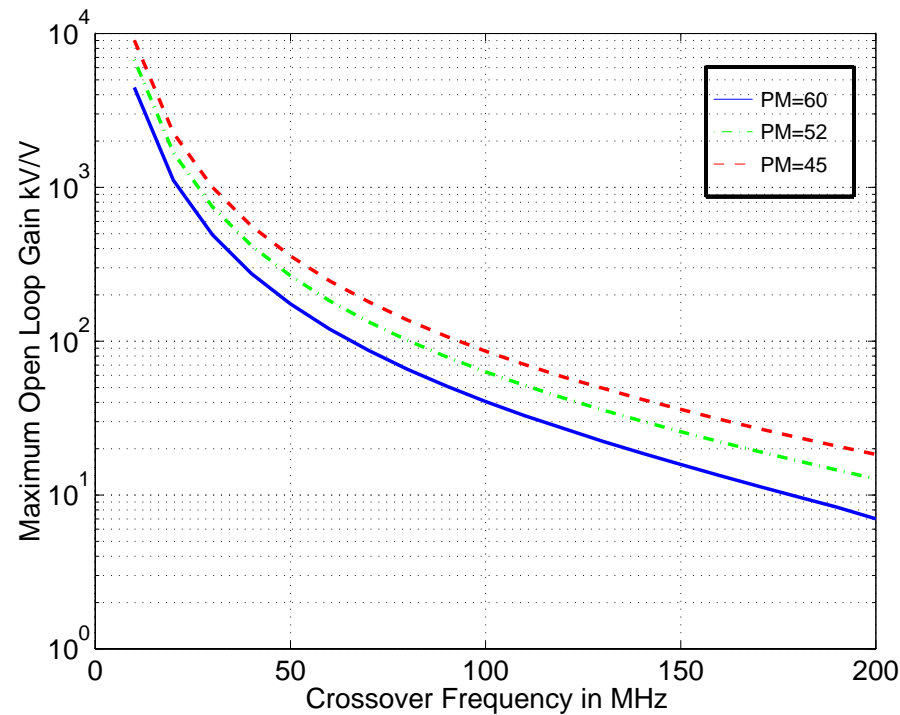

Maximum gain versus unity gain frequency for different phase margins




Optimal Trade-off Curves (IV)

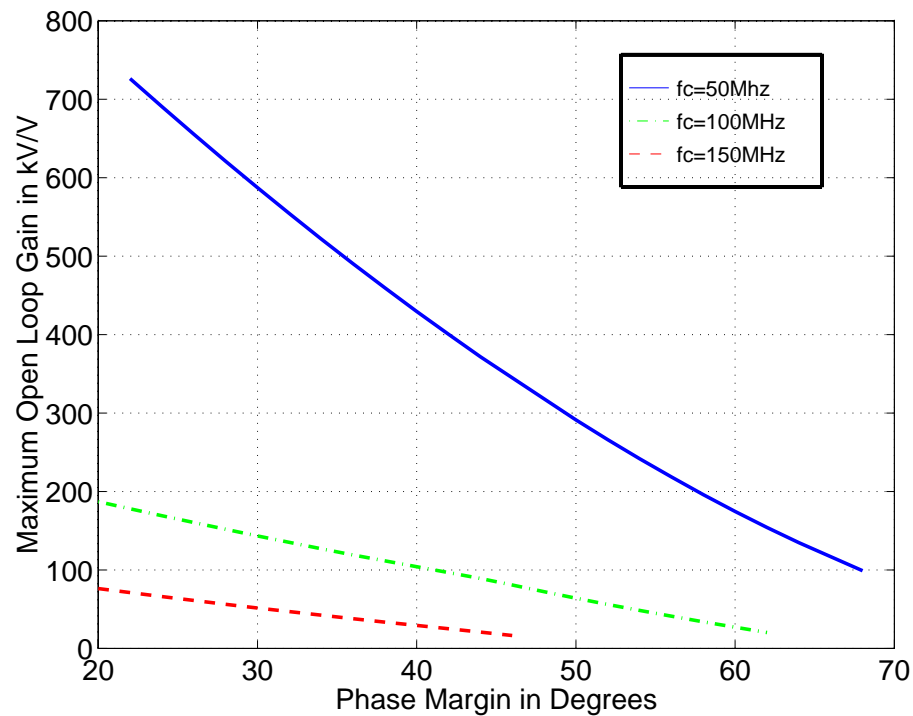


Maximum open loop gain versus phase margin for different unity gain frequencies



Optimal Trade-off Curves (V)

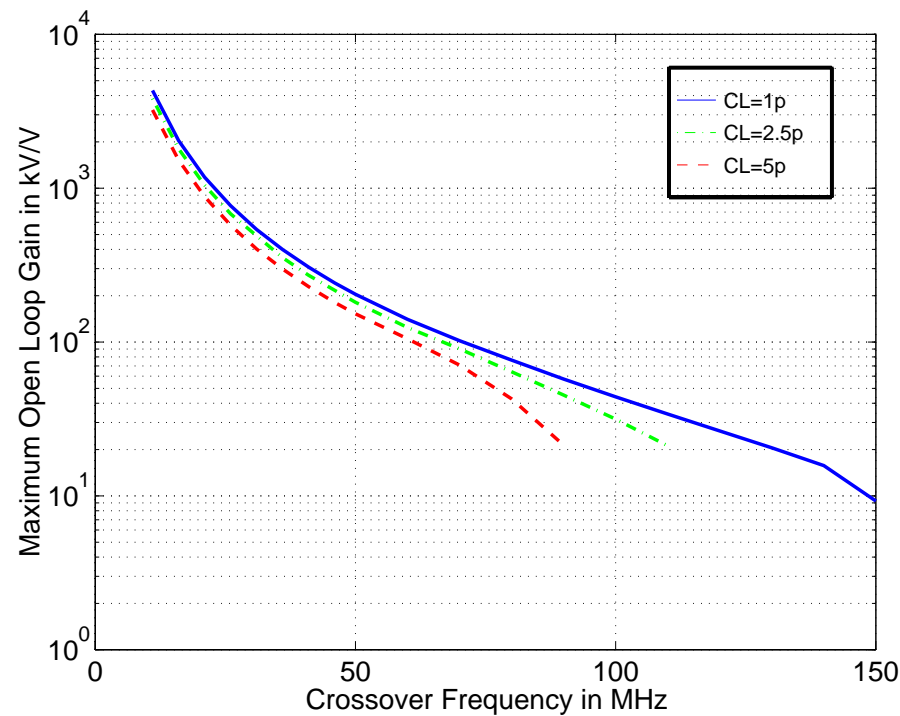

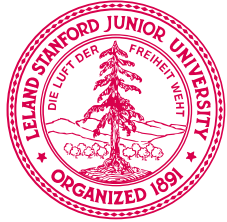Maximum open loop gain versus unity gain frequency for different load capacitances



Conclusions

Geometric Programming problems

- Arise in *many* important *analog circuit* design problems, in particular *CMOS op-amp* design.
- Can be (*globally, efficiently*) *solved*.

We can

- *automatically, directly from specifications, optimally design* CMOS op-amps.



Acknowledgments

We gratefully acknowledge Edo Walks, who wrote the geometric programming code.



Final thought ...

... the great watershed in optimization isn't between linearity and nonlinearity, but convexity and nonconvexity.

— R. Rockafellar, SIAM Review 1993