

# **Power Amplifier Linearization Techniques: An Overview**


**Workshop on RF Circuits for 2.5G  
and 3G Wireless Systems  
February 4, 2001**



*Joel L. Dawson*  
*Ph.D. Candidate, Stanford University*

# List of Topics

- Motivation for using linearization
- Linearization as a theoretical problem
- Survey of commonly employed techniques

# Linearity vs. Power Efficiency

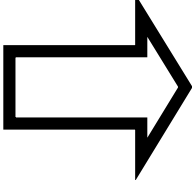*Power efficiency*  *Battery lifetime*  
*Thermal management*

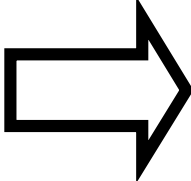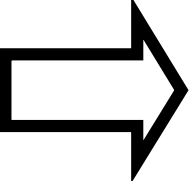
*Linearity*  **Sophisticated  
Modulation  
Techniques**  *Spectral efficiency*

# PA Tradeoffs

- **Power Efficiency => Switching PA's  
(class D, E, F)**
- **Linearity => Class A, AB, B, C.**
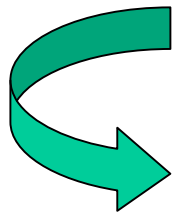
# Can nonlinear system theory help?

Theory of **time-invariant** (or, “stationary”) nonlinear systems is well-developed.




Volterra series, Weiner systems,  
Hammerstein systems...


**Problem:** *Intensely* formal, and usually lacks the conceptual clarity that leads to design insight.

# Example: 3<sup>rd</sup> order nonlinearity in a two-tone experiment

The input tones:


$$2\alpha \cos \omega_1 t + 2\beta \cos \omega_2 t$$
$$\alpha e^{j\omega_1 t}, \alpha e^{-j\omega_1 t}, \beta e^{j\omega_2 t}, \beta e^{-j\omega_2 t}$$

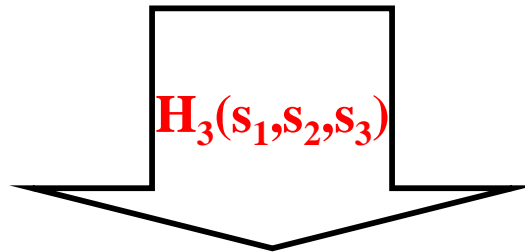Output sinusoids at:  $3\omega_1, 3\omega_2, 2\omega_1 - \omega_2, 2\omega_2 - \omega_1, 2\omega_1 + \omega_2, 2\omega_2 + \omega_1$



An output product:  $\alpha^2 \beta H_3(j\omega_1, j\omega_1, -j\omega_2) e^{j(2\omega_1 - \omega_2)t}$

# So where does the theory leave us?

- Odd order nonlinearities cause distortion products that are in-band.
- Outrageous behavior in the lab may imply that the device under test is *not* time-invariant.

# Design implications:


- An important measure of the strength of a given linearization method is its robustness to poor characterization of the PA.
- Design, if possible, to “force” PA to behave as a benign nonlinear system (e.g., look for ways to preserve time-invariance).


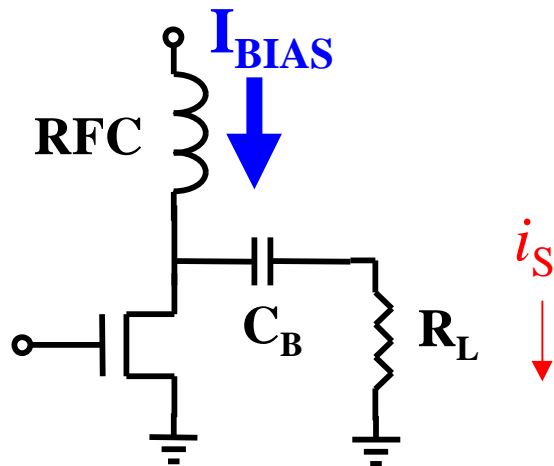
# Technique I: Power Backoff


For “small” inputs,  
this term is dominant.

**Basic principle:**  $V_o(x) = a_0 + a_1x + a_2x^2 + \dots = \sum_{n=0}^{\infty} a_n x^n$




$|I_{BIAS}| \gg |i_S|$   
**Low efficiency**

# Power Backoff, cont.

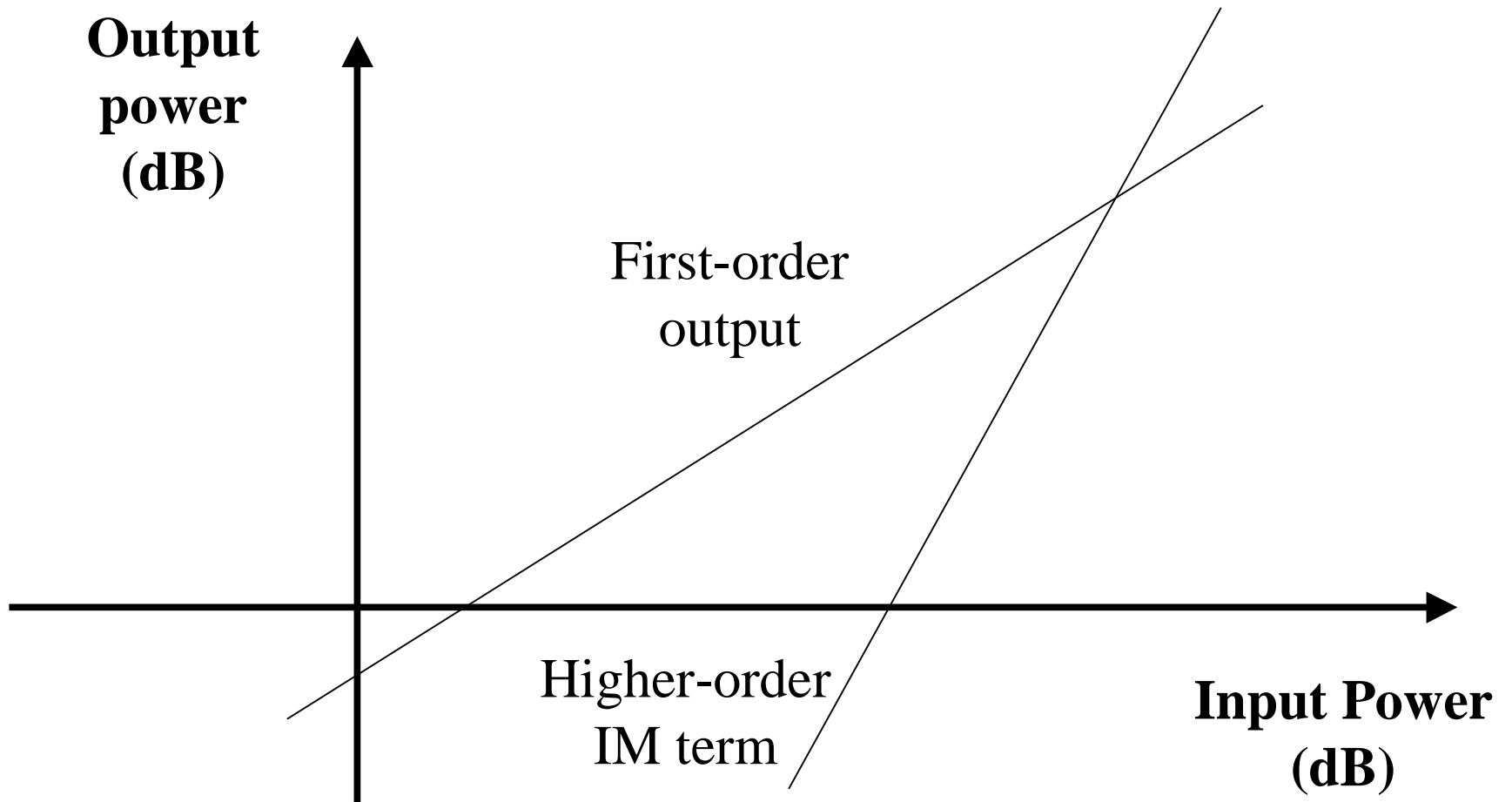

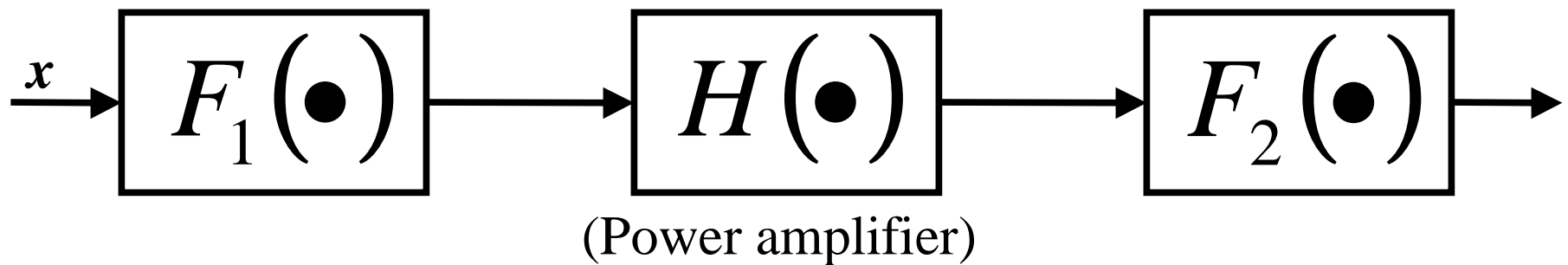
# Corrective distortion: predistortion and/or postdistortion



Most general problem: choose  $F_1$  and  $F_2$  such that  $F_2(H(F_1(x)))$  is a linear function of the input variable  $x$ .


# Technique II: **Predistortion**

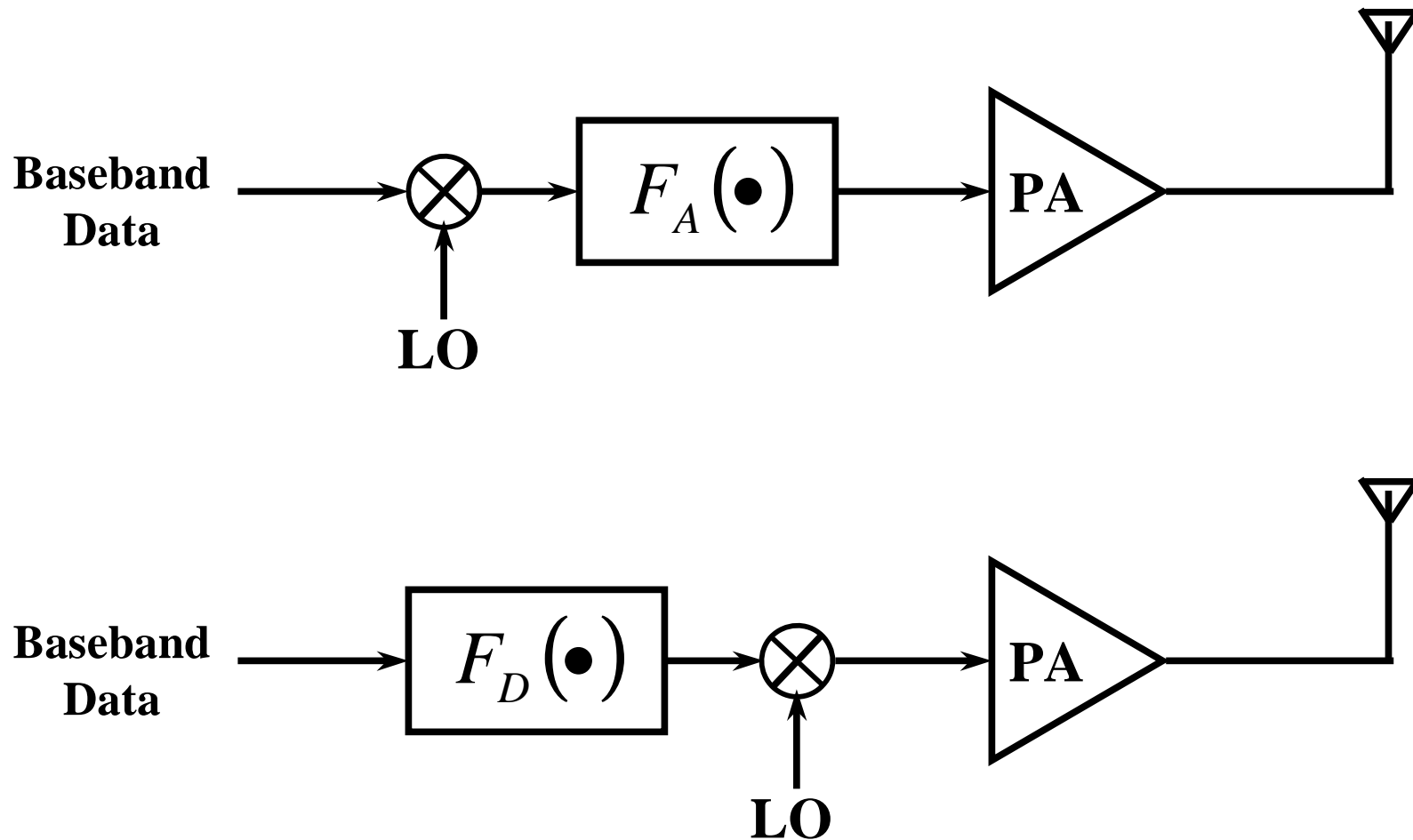

## **Key design issues for a predistorter:**

- In analog case, how to realize the predistortion function.
- Initial calibration or training.
- Sensitive to drift.

# Technique III: Adaptive Predistortion

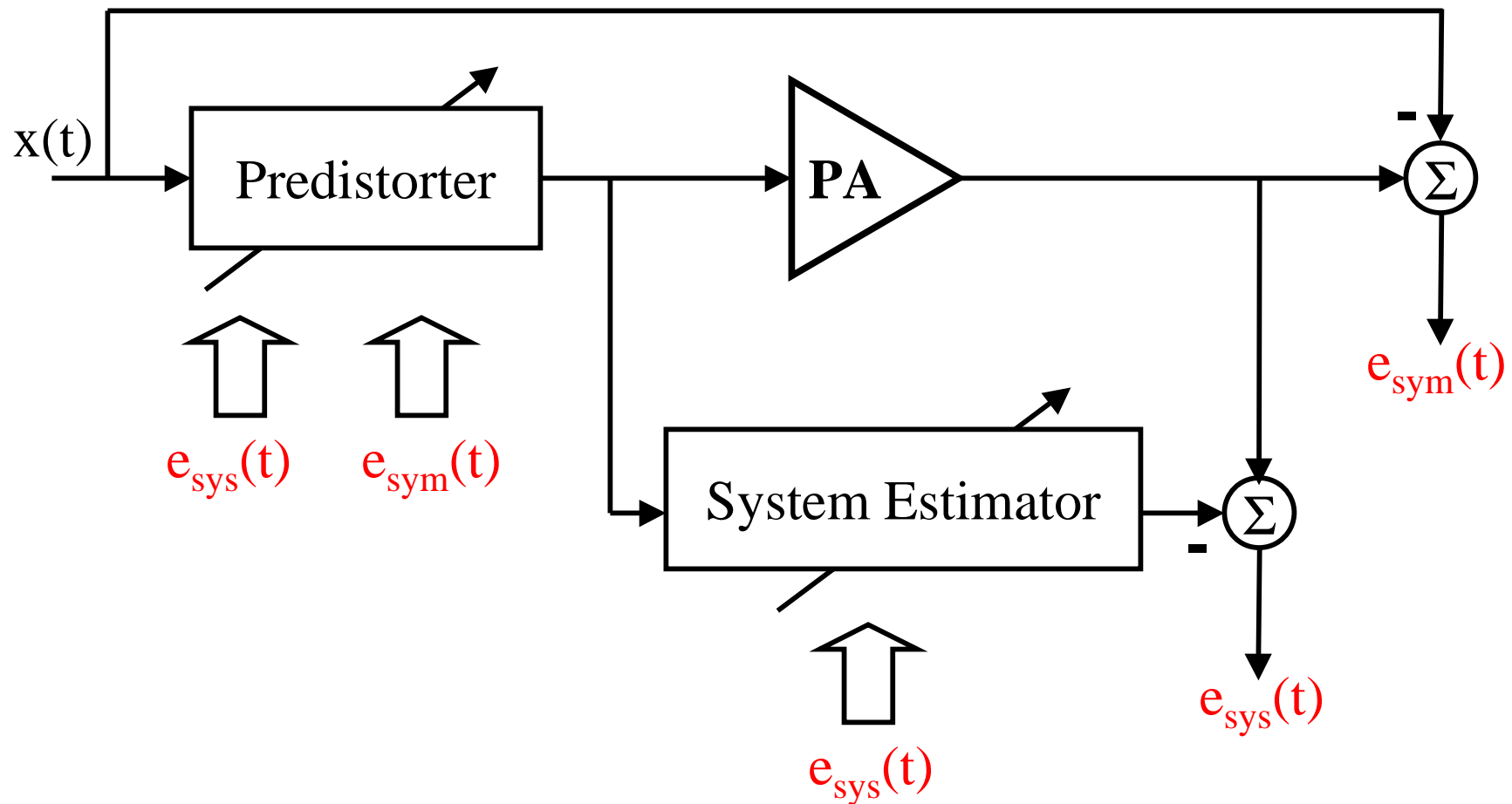

# **Adaptive Predistortion: advantages**


- Does not suffer the bandwidth limitation incurred by continuous-feedback techniques.
- Solves the problem of drift sensitivity.

# Adaptive Predistortion: design issues

- New, discrete-time feedback stability problem associated with model estimation.
- Depends on having a good power amplifier model.
- Complexity: incurs power overhead of a DSP chip.



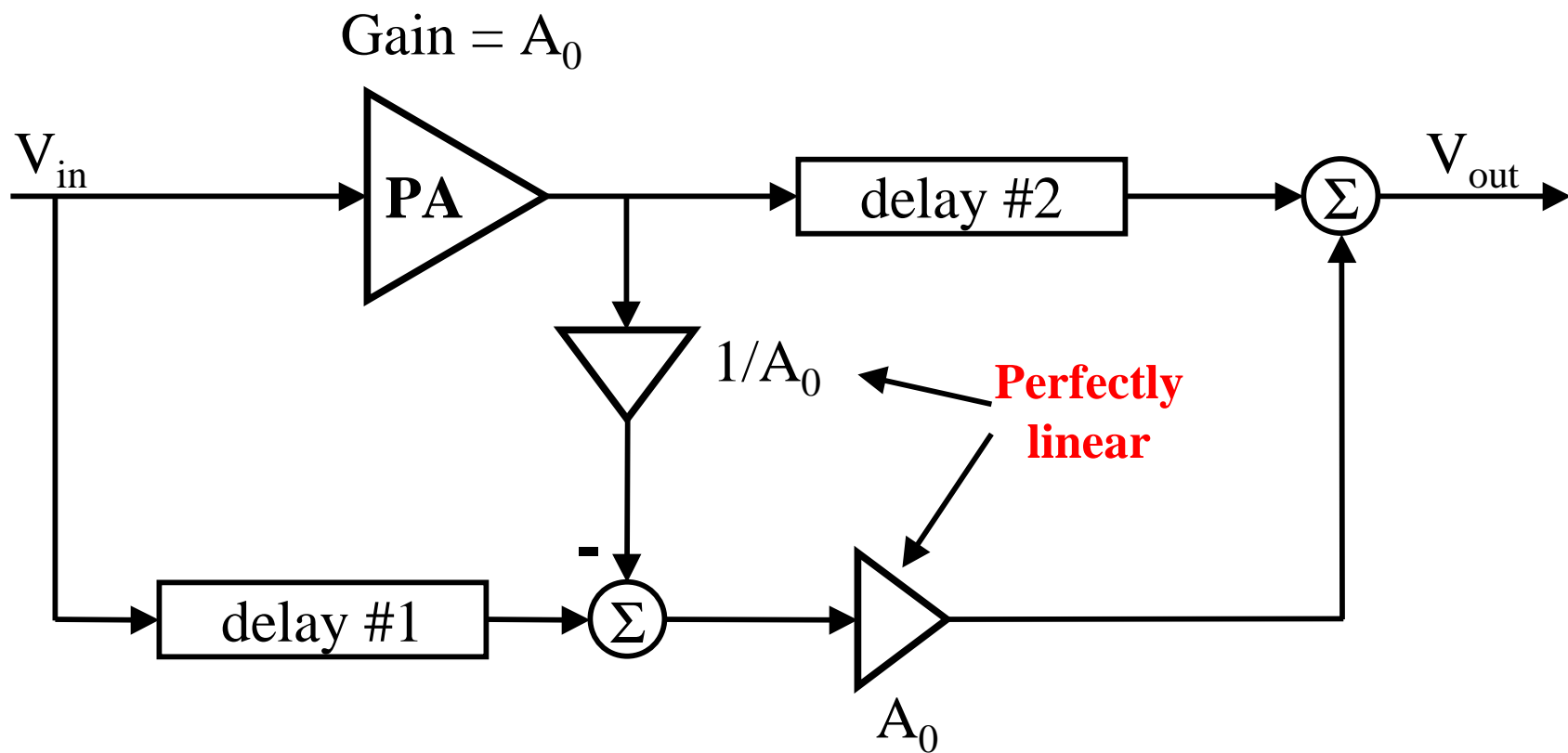
# Technique IV: Feedforward Linearization



# **Feedforward: stable, but...**

- Matching delay lines, amplifier gains not trivial.
- Susceptible to drift and aging.
- Low-loss delay lines, summations critical.
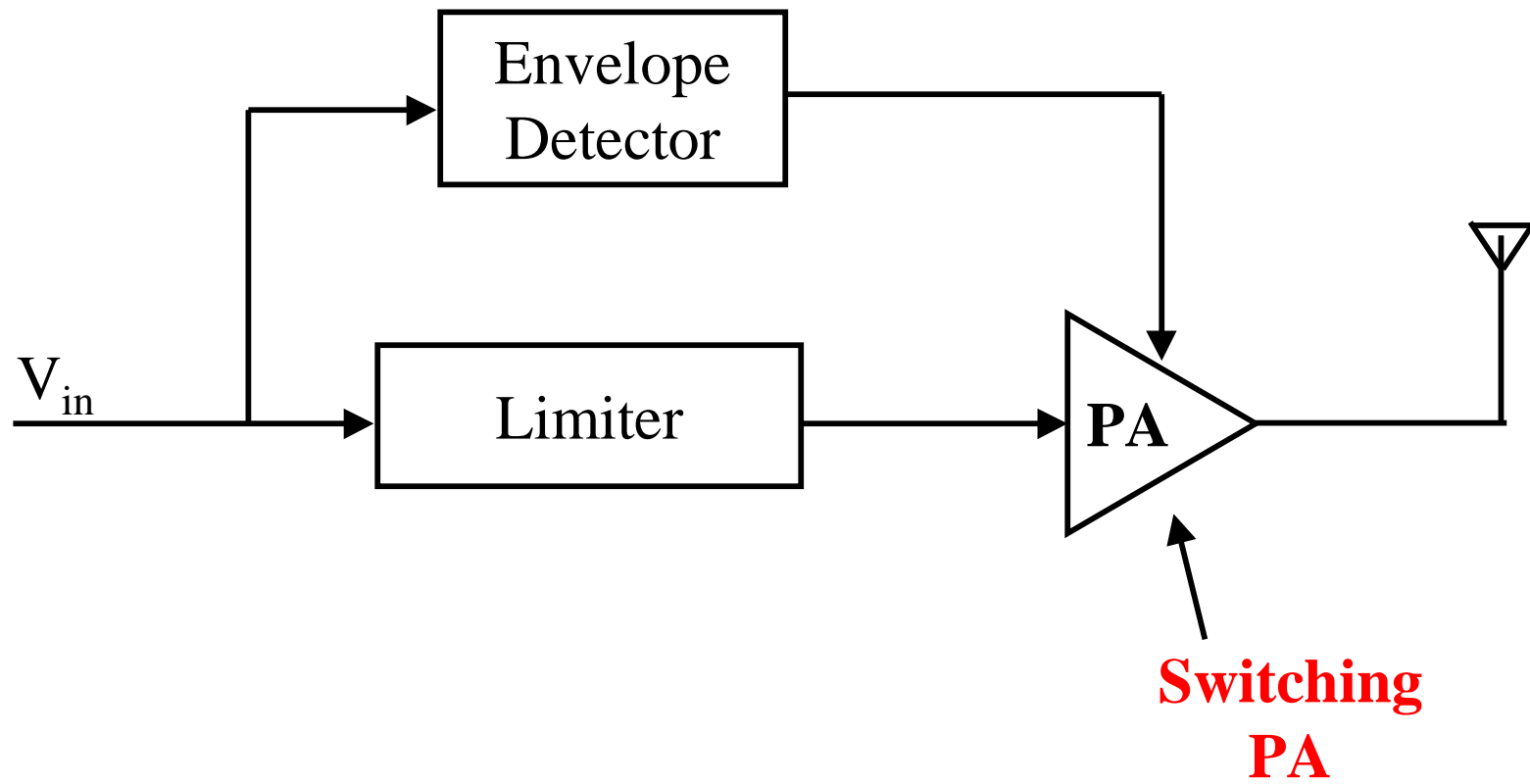
# Technique V: Envelope Elimination and Restoration




# EER design issues

- Phase matching between the two signal paths critical.
- Polar feedback a possibility.
- Restoring the envelope in a power-efficient way is very challenging.
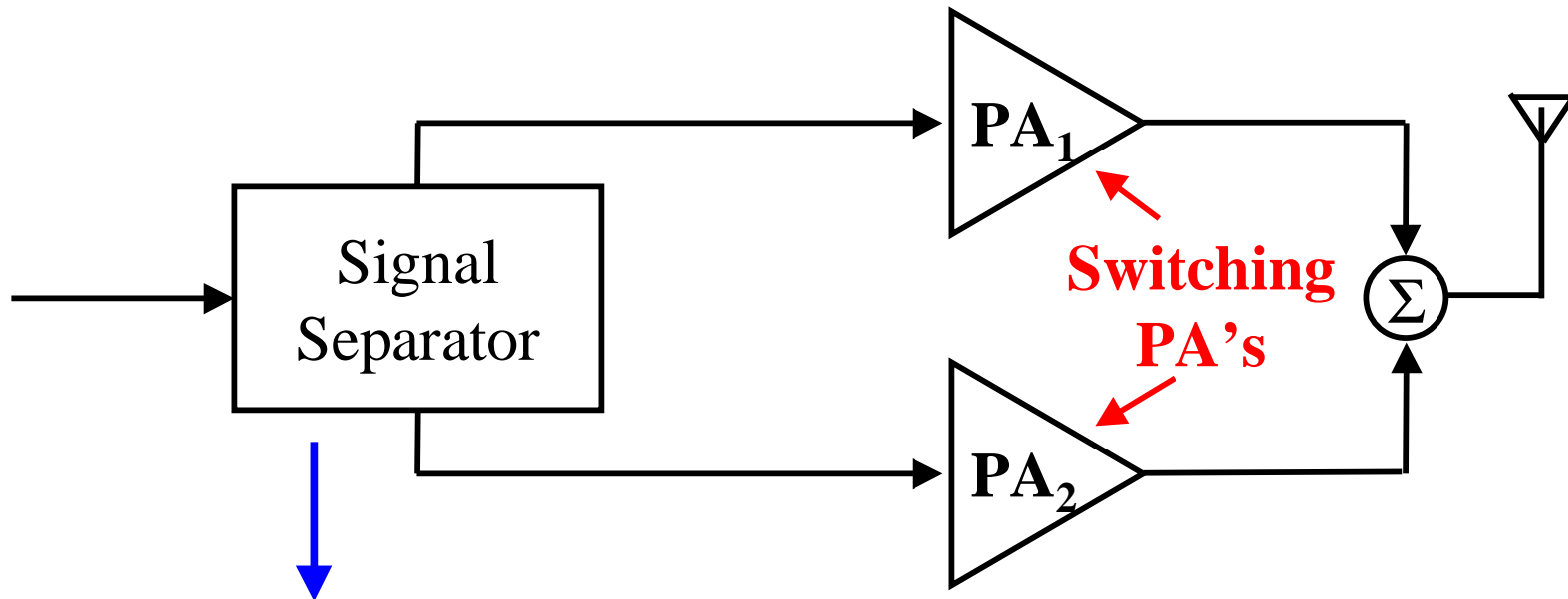
# Technique VI: LINC

*Linear* amplification with *Nonlinear* Components



$$a(t) \cos[\omega_c t + \phi(t)] = 0.5V_0 \sin[\omega_c t + \phi(t) + \theta(t)] - 0.5V_0 \sin[\omega_c t + \phi(t) + \theta(t)]$$


**Constant-amplitude terms**

$$\theta(t) = \sin^{-1} \left[ \frac{a(t)}{V_0} \right]$$



# LINC design issues

- Signal separation complicated, but possible.
- Good power combining with *low loss and high isolation* is the key barrier.

# Technique VII: Cartesian Feedback

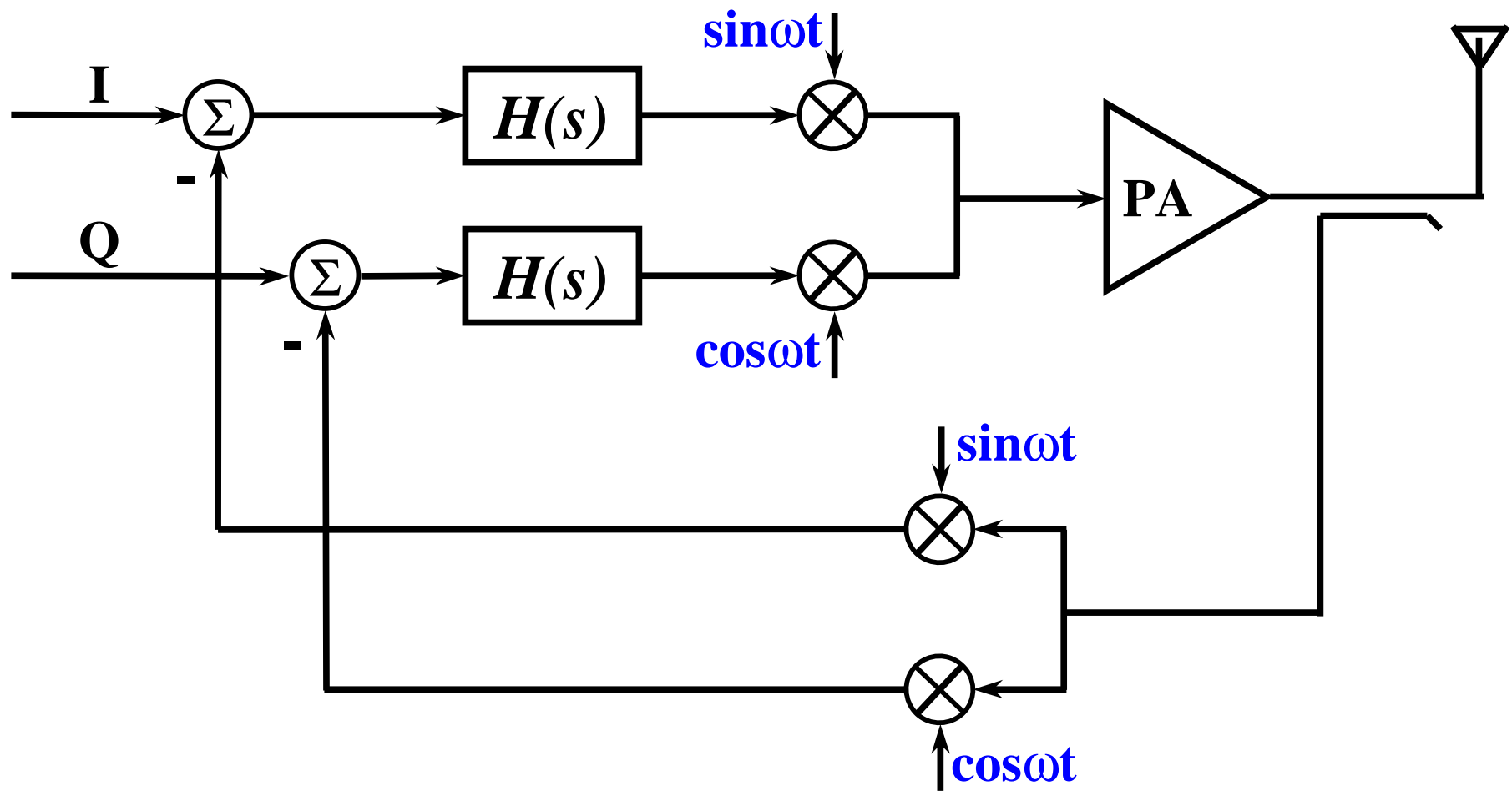
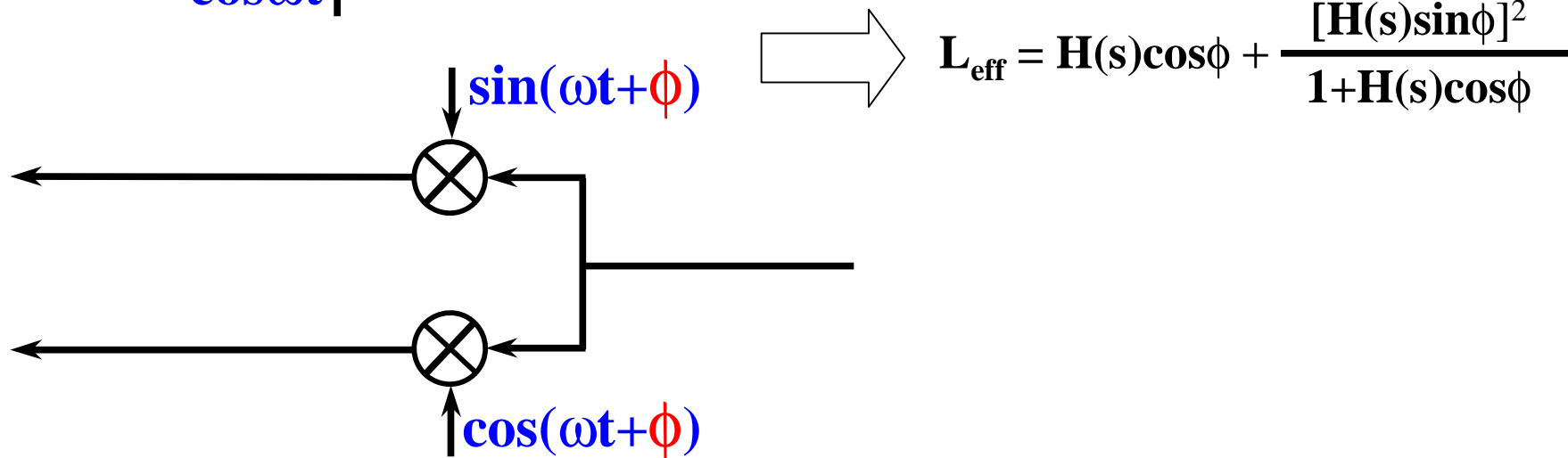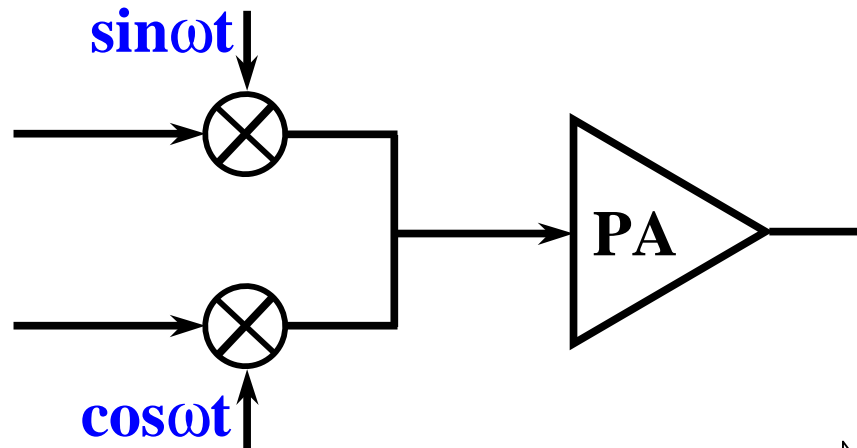
# Major design consideration in CFB systems: phase alignment





# CFB Strengths and Weaknesses

- **W**: Bandwidth limitation
- **W**: Stability concerns
  
- **S**: Low-complexity
- **S**: Highly resistant to drift and aging
- **SS**: Robust to poor characterization of PA

# Summary

- **Power Backoff:** simplicity; low power efficiency.
- **Predistortion:** conceptually clear; requires good PA model.
- **Adaptive Predistortion:** No drift problem; introduces complexity.
- **Feedforward:** No stability worries; matching and drift concerns.
- **EER:** Possibly high-efficiency; adds another “power amp” problem.
- **LINC:** Conceptually appealing; fundamental implementation issues.
- **CFB:** simplicity, robust to poor PA model; stability concerns.

**Copies of these slides...**

**<http://smirc.stanford.edu>**

**Available at the conclusion of ISSCC 2001.**